

INDIAN INSTITUTE OF INFORMATION TECHNOLOGY VADODARA - INTERNATIONAL CAMPUS DIU



Practical Work

Name : Pooja
Roll No : 202311063
Subject : Computer Organisation and Architecture
Course : CS268
Branch : CSE
Batch : 2023 - 2027

EXPERIMENT-8

Aim:- Design and implementation of an advance pipeline architecture in verilog.

Prerequisites:- A fair understanding of pipeline concept and verilog language.

Theory:- It is four stage pipeline:-

1. **Stage 1 (Instruction Fetch/Decode):** Fetches operands from a register bank and decodes the instruction inputs (e.g., source registers, function code, destination register, and memory address).
2. **Stage 2 (Execution):** Performs the specified operation (e.g., addition, subtraction, multiplication) based on a function code.
3. **Stage 3 (Destination Register):** Writes the execution result back to the specified register in the register bank.
4. **Stage 4 (Write Back):** Stores the result in a memory bank at the specified address.

To avoid overlapping of consecutive stages two clock signal are used as shown:-


 


Fig.-1

Clocking Issue in Pipeline

 - It is important that the consecutive stages be applied suitable clocks for correct operation.
- Two options:
 - a) Use master/slave flip-flops in the latches to avoid race condition.
 - b) Use non-overlapping two-phase clock for the consecutive pipeline stages.



Main code:-

C:/Users/pooja/project_5/project_5.srscs/sources_1/new/pipe.v

```
1  module pipe(zout,rs1,rs2,rd,func,addr,clk1,clk2);
2  input[3:0] rs1,rs2,rd;
3  input clk1,clk2;
4  input [3:0] func;
5  input [7:0] addr;
6  output [15:0] zout;
7  reg [15:0] l1a,l1b,l2z,l3z;
8  reg [7:0] l1add,l2add,l3add;
9  reg [3:0] l1func,l1rd,l2rd;
10 reg [15:0] regbank [15:0];
11 reg [15:0] membank[255:0];
12
13 assign zout=l3z;
14 always @(posedge clk1)
15 begin
16 l1a <= #2 regbank[rs1];
17 l1b <= #2 regbank[rs2];
18 l1func <= #2 func;
19 l1rd <= #2 rd;
20 l1add <= #2 addr;
21 end
22 always @(posedge clk2) begin
23 case(func)
24 0: l2z <= #2 l1a+l1b;
25 1: l2z <= #2 l1a-l1b;
26 2: l2z <= #2 l1a*l1b;
27 3: l2z <= #2 l1a;
28 4: l2z <= #2 l1b;
29 5: l2z <= #2 l1a&l1b;
30 6: l2z <= #2 l1a|l1b;
31 7: l2z <= #2 l1a^l1b;
32 8: l2z <= #2 ~l1a;
33 9: l2z <= #2 ~l1b;
34 10: l2z <= #2 l1a>>1;
35 11: l2z <= #2 l1b<<1;
36 default: l2z<=16'hxxx; endcase
37 l2rd <= #2 l1rd;
38 l2add <= #2 l1add;
39 end
40 always @(posedge clk1)
41 begin
42 regbank[l2rd] <=#2 l2z;
43 l3z <=#2 l2z;
44 l3add <=#2 l2add;
45 end
46 always @(posedge clk2) begin
47 membank[l3add]=#2 l3z; end
48 endmodule
```

Testbench code:-

C:/Users/pooja/project_5/project_5.srsc/sim_1/new/pipe_tb.v

```

1 module simuli();
2   reg[3:0] rs1;
3   reg[3:0] rs2;
4   reg[3:0] rd;
5   reg[3:0] func;
6   reg[7:0] addr;
7   wire [15:0] zout;
8   integer k, i;
9   reg clk1, clk2;
10  pipe pipe(zout,rs1,rs2,rd,func,addr,clk1,clk2);
11  initial clk1=1;
12  initial clk2=0;
13  always #10 clk1=~clk1;
14  always #10 clk2=~clk2;
15  initial
16  for(k=0;k<15;k=k+1)
17  begin
18    pipe.regbank[k]=k;
19  end
20  initial begin
21    $dumpfile("pipe.vcd");
22    $dumpvars;
23    #20 rs1=6; rs2=1; rd=10; addr= 125; k=addr; func = 2; #20 rs1=9; rs2=8; rd=12; addr=126;k=addr;
24    func = 3; #20 rs1=2; rs2=4; rd=13; addr= 125;k=addr; func = 4; #60 $finish ;
25  end
26 endmodule

```

GTK Waveform:-



